


Pre-Laboratory Worksheet
Experiment NE04 - RC Circuit
Department of Physics
The University of Hong Kong

Name: _____ Student ID: _____ Date: _____

Remark: Please submit Pre-Laboratory Worksheet to laboratory technician when you arrive the laboratory

Background information:

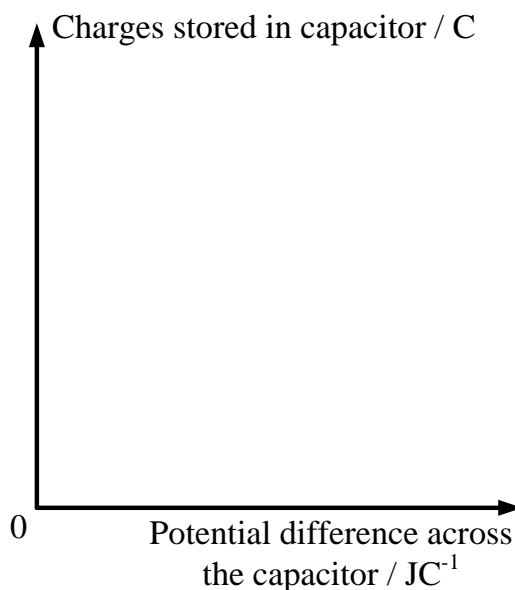1. According to equation (1) in the lab manual, sketch the curve of charges stored in capacitor vs. the potential difference across the capacitor. What is the relationship between the charges stored in capacitor and potential difference across the capacitor?
Also state the physical meanings of the slope of the curve and the area under the curve. (Hints: Unit of potential difference across the capacitor is $J C^{-1}$.)



2. What is the physical meaning of the current vs. time graph in Experiment 2:

3. Use the equations in the lab manual to complete the following table:

Suggested solution:

Charging				
	Charge stored in capacitor	Current of the circuit	p.d. across capacitor	p.d. across resistor
Time	$Q(t) = CV_s \left(1 - e^{-\frac{t}{RC}} \right)$	$I(t) = \frac{V_s}{R} e^{-\frac{t}{RC}}$	$V_C(t) = V_s \left(1 - e^{-\frac{t}{RC}} \right)$	$V_R(t) = V_s e^{-\frac{t}{RC}}$
$t = 0$	$Q(t = 0) =$	$I(t = 0) =$	$V_C(t = 0) =$	$V_R(t = 0) =$
$t \rightarrow \infty$	$Q(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} CV_s \left(1 - e^{-\frac{t}{RC}} \right)$ $=$	$I(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} \frac{V_s}{R} e^{-\frac{t}{RC}}$ $=$	$V_C(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} V_s \left(1 - e^{-\frac{t}{RC}} \right)$ $=$	$V_R(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} V_s e^{-\frac{t}{RC}}$ $=$

Discharging				
	Charge stored in capacitor	Current of the circuit	p.d. across capacitor	p.d. across resistor
Time	$Q(t) = CV_s e^{-\frac{t}{RC}}$	$I(t) = -\frac{V_s}{R} e^{-\frac{t}{RC}}$	$V_C(t) = V_s e^{-\frac{t}{RC}}$	$V_R(t) = V_s e^{-\frac{t}{RC}}$
$t = 0$	$Q(t = 0) =$	$I(t = 0) =$	$V_C(t = 0) =$	$V_R(t = 0) =$
$t \rightarrow \infty$	$Q(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} CV_s e^{-\frac{t}{RC}}$ $=$	$I(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} \frac{V_s}{R} e^{-\frac{t}{RC}}$ $=$	$V_C(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} V_s e^{-\frac{t}{RC}}$ $=$	$V_R(t \rightarrow \infty)$ $= \lim_{t \rightarrow \infty} V_s e^{-\frac{t}{RC}}$ $=$

4. Use the equations of potential difference across capacitor and resistor during charging and discharging to complete the following table. Note that the values of potential difference across capacitor and resistor should be in terms of the electromotive force V_s with 2 decimal places.

Time	Charging		Discharging	
	$V_C(t) = V_s \left(1 - e^{-\frac{t}{RC}} \right)$	$V_R(t) = V_s e^{-\frac{t}{RC}}$	$V_C(t) = V_s e^{-\frac{t}{RC}}$	$V_R(t) = V_s e^{-\frac{t}{RC}}$
$t = \tau = RC$				
$t = 2\tau = 2RC$				
$t = 3\tau = 3RC$				
$t = 4\tau = 4RC$				
$t = 5\tau = 5RC$				
$t = 6\tau = 6RC$				

5. In practice, if the potential difference across the resistor is equal to 0.674% ε , the capacitor could be considered as either completely charged or completely discharged. The completely charging time or completely discharging time is called *transient response time*. From the table in pre-lab question 4. What is the *transient response time* in terms on RC ?

Transient response time: _____

6. What is the unit of time constant? And complete the following table.

The unit of time constant is _____

Capacitor	Resistor	Theoretical time constant	Transient response time (Definition: see Prelab Q.5)
1.0F	10 Ω		
1.0F	33 Ω		
1.0F	100 Ω		

7. Label in the x-axis of the following graphs to indicate the *time constant* of a charging RC circuit

